

SHEET-2

N -33MM, P -33MM

Parameters:

$$V_{dd}=1.8v$$

$$\text{Gain}=60.1\text{DB}$$

$$\text{PM}= 41.1$$

$$\text{BW}= 1.34\text{MHz}$$

$$\text{Power}= 24.9\mu\text{W}$$

$$\text{Current}= 13.8\mu\text{A}$$

$$\text{CMRR}=93.8\text{DB}$$

$$\text{PSRR}=104.6\text{DB}$$

$$\text{SR}=3\text{V}/\mu\text{S}$$

$$C_L=342.7\text{KpF}$$

$$V_{th}(\text{nmos})=0.33v - 0.34v$$

$$V_{th}(\text{pmos})=0.43v$$

$$\mu_n\text{cox}=345\mu\text{A}/\text{V}^2$$

$$\mu_p\text{cox}=55\mu\text{A}/\text{V}^2$$

Calculation:

$$\text{SR}=\frac{I}{C_c}$$

$$I_5=\text{SR}*\text{C}_c$$

$$I_5=0.1p \times 3\text{V}/\mu\text{S}$$

$$=0.3\mu\text{A}$$

$$V_{DS5}=V_{GS5}-V_{TH}$$

$$=V_{dd}-V_{bias}-V_{th}$$

$$=1.8-1.246-0.43$$

$$V_{ds5}=0.124V$$

$$i) \left(\frac{W}{L}\right)_5 = \frac{2 \cdot I_5}{\mu_{pcox} (v_{ds5})^2} = \frac{2(0.3u)}{55u \cdot (0.124)^2} = 0.709$$

$$\text{Practical : } \frac{240n}{340n} = 0.705$$

$$\text{Theoretical: } W_5=244n \quad L_5=344n$$

$$ii) \quad W_{GB} = \frac{gm_1}{c_c}$$

$$Gm_1 = W_{GB} \cdot C_c = (0.1p)(20M) = 2u \text{ mho}$$

$$\left(\frac{W}{L}\right)_1 = \frac{gm_1^2}{2kpI_1} = \frac{(2u)^2}{2 \cdot 55u \cdot 0.15u} = 0.24$$

$$\text{Practical : } \frac{240n}{1u} = 0.24$$

$$\text{Theoretical: } \frac{240n=0.24}{1u} W_1=240n \quad L_1=1u$$

$$(iii) \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 0.24$$

$$W_2=240n$$

$$L_2=1\mu$$

$$(iv) \left(\frac{W}{L}\right)_3 = \frac{2 \cdot i_3}{\mu_{ncox} [V_{ds3}]^2} = \frac{2 \times 0.15u}{345u \times 0.035^2} = 0.709 V_{ds3} = V_{gs3} - V_{ss}$$

$$=V_{dd} - V_{bias} - 0 = 1.8 - 1.765 = 0.035$$

$$w_3=244n ; L_3=344n$$

$$(v) \left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 = 0.709$$

$$V_{ds3} = V_{ds6}$$

$$(vi) g_{m6} = \frac{gm_2}{\tan\left(\frac{90-PM}{2}\right)} = \frac{2u}{\tan\left(\frac{90-41.1}{2}\right)} = 4.39u$$

$$\left(\frac{W}{L}\right)_6 = \frac{Gm_6}{\mu n C_{ox} [V_{ds6}]^2} = \frac{4.39u}{345u * 0.035^2} = 0.363$$

$$W_6 = 180n$$

$$L_6 = 500n$$

$$(vii) I_6 = \frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_3} * I_3 = \frac{0.036}{0.709} * 0.15u = 0.07uA$$

$$I_6 = I_7$$

$$\left(\frac{W}{L}\right)_7 = \frac{I_7}{I_5} * \left(\frac{W}{L}\right)_5$$

$$\left(\frac{W}{L}\right)_7 = \frac{0.07u}{0.3u} * 0.709 = 0.165$$

$$W_7 = 100n$$

$$L_7 = 590n$$

$$(viii) \left(\frac{W}{L}\right)_{10} = \frac{2 * I_{10}}{\mu p c_{ox} (V_{gs10} - V_{th})^2}$$

$$\text{Assume } I_{10} = 1u; \left(\frac{W}{L}\right)_{10} = \frac{2 * 1u}{55u (0.19)^2} = 1 \quad V_{ds10} = V_{gs10} - V_{th} = 1.8 - V_{bias} - 0.43$$

$$= 1.8 - 1.18 - 0.43 = 0.19$$

$$W_{10} = 340n$$

$$L_{10} = 340n$$

$$(ix) \left(\frac{W}{L}\right)_9 = \left(\frac{W}{L}\right)_{10} = 1$$

$$W_9 = 340n ; L_9 = 340n$$

$$(x) R_0 = \sqrt{\frac{1}{2Kp \left(\frac{W}{L}\right)_8 I_8}}$$

$$\text{Let } R_0 = 390k\Omega , I_8 = 1u$$

$$\left(\frac{W}{L}\right)_8 = \frac{1}{2kp R_0^2 I_8} = 0.059$$

$$W_8 = 239n , L_8 = 4u$$

TABLE:

Simualted Results :

	M1	M2	M3	M4	M5	M6	M7	M8	M9	M10
W	240n	280n	340n							
L	1u	1u	340n	340n	340n	340n	500n	4u	500n	340n

Theoretical values :

	M1	M2	M3	M4	M5	M6	M7	M8	M9	M10
W	240n	240n	244n	244n	244n	230n	180n	100n	340n	340n
L	1u	1u	344n	344n	344n	6.5u	500n	590n	340n	340n

